

Circuits II practical project

By:

- * Ziad Mohamed Ayman 43-4384**
- * Nadine Ahmed Abdelaziz 43-4385**
- * Maryam Ahmed Saad 43-14354**

Tutorial: T5 IET

Circuit Type:

Non-inverting low pass filter

Supervised by:

Nada Ayman

The components we used are :

- * 1X Amplifier LM324
- * 1X 1nF Capacitor
- * 1X 16k Ω Resistor
- * 2x 10k Ω Resistor
- * 1X VAC
- * 2X VDC (20V)
- * 1X VDC (10V)

1-We chose $F_o = 10\text{KHz}$ & $C=1\text{nF}$
Accordingly $R=1/2\pi F_o C \approx 16\text{k}\Omega$

2- We chose Gain $A= 2$
Accordingly $R_2/R_3=1$
 $R_2/R_3=1 \rightarrow R_2=R_3=10\text{k}\Omega$

13 / 27

NONINVERTING


$F_o = 1/(2\pi R_1 C_1)$

Gain = $1 + R_3/R_2$


Figure 13. Low-Pass Filter Circuits

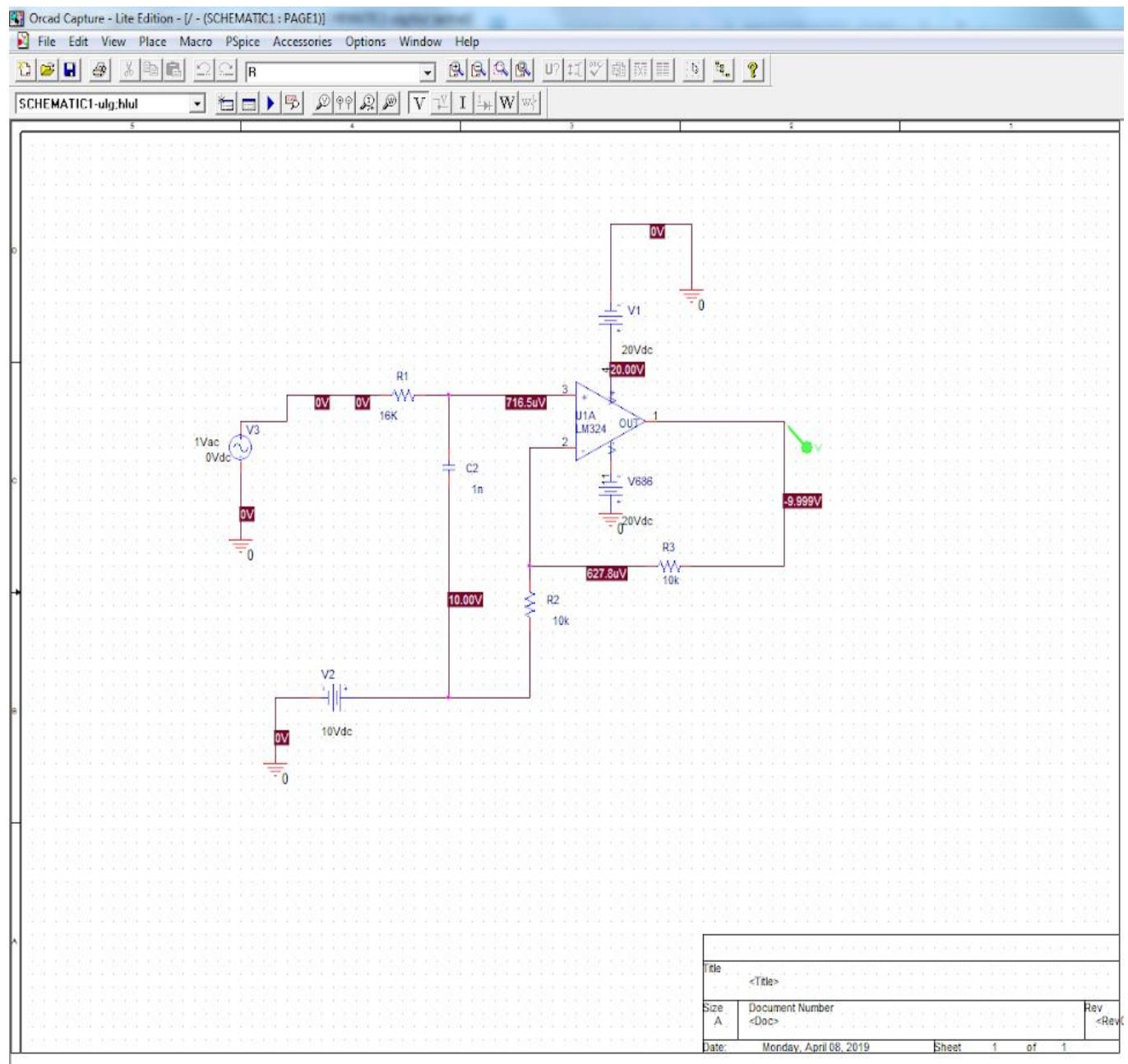3.1.2 High Pass Filter Circuits

Typical high-pass filter circuits are shown in Figure 14.



AT Fo --> $V = V_m / \sqrt{2}$

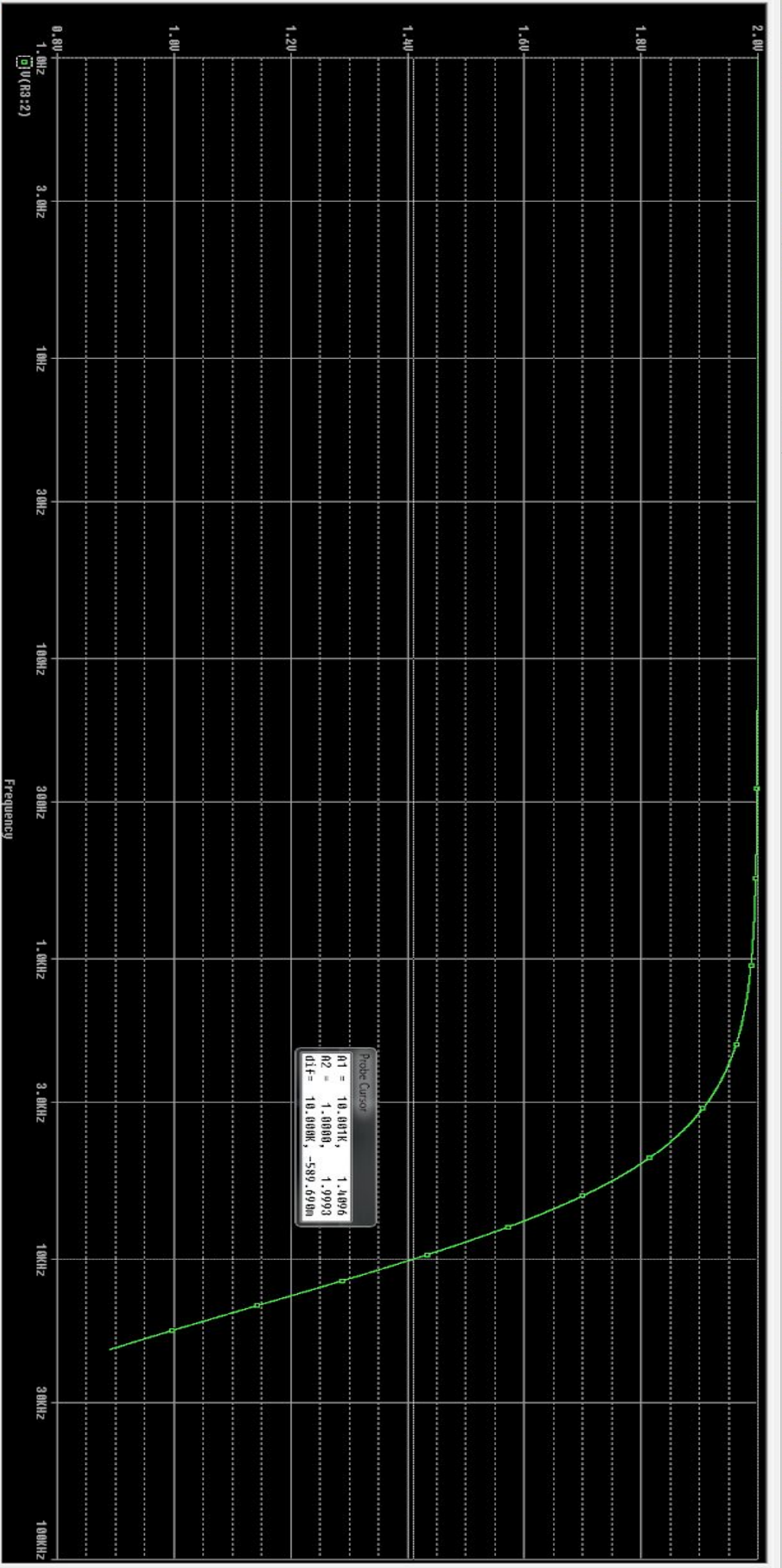

99999999

Profile: "SCHEMATIC" [C:\Program Files\National Instruments\LabVIEW\bin\SCHEMATIC.vi] [C:\Program Files\National Instruments\LabVIEW\bin\SCHEMATIC.vi]
 Reading and checking circuit
 Circuit read in and checked, no errors
 Calculating bias point
 Bias point calculated
 AC level noise analysis
 AC analysis finished
 Simulation complete

Start = 1
 Freq = 20.00E+03
 End = 20.00E+03

Analysis View Devices

Freq = 20.00E+03

100%